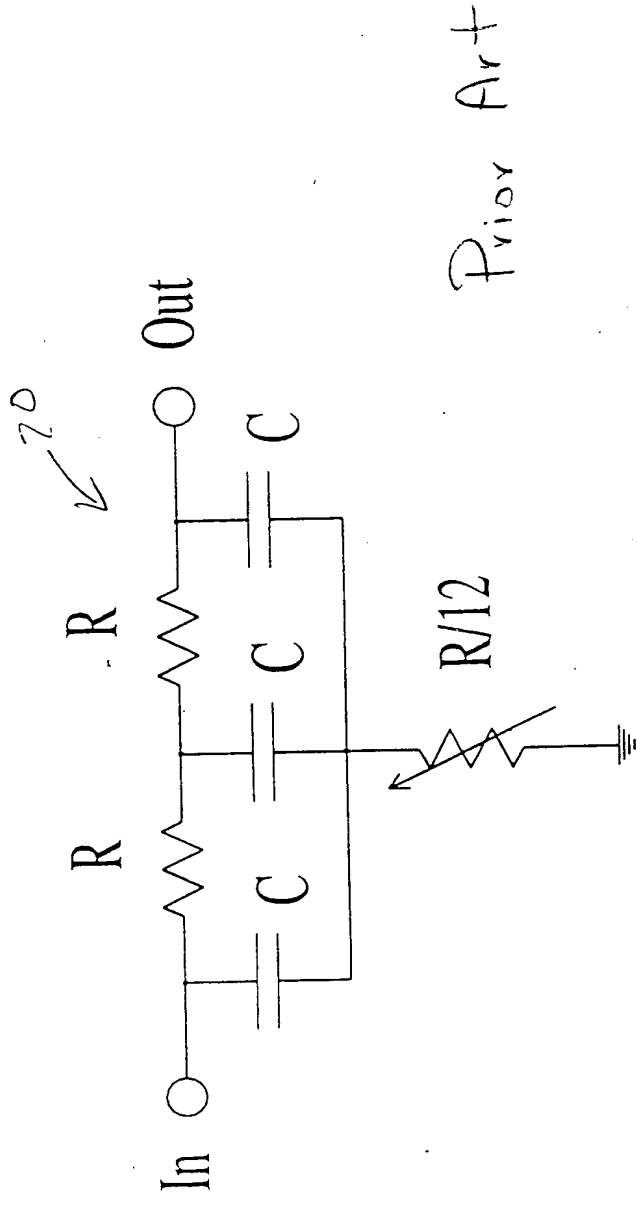


003327 00334260




$$G(s) = \frac{(RCs)^3 + 4(RCs)^2 + 3RCs + 12}{(RCs)^3 + 16(RCs)^2 + 39RCs + 12}$$

$$f(\text{null}) = \sqrt[3]{3} / (2\pi RC)$$

Figure 1

Isolated-Integrator Band-Reject Filter

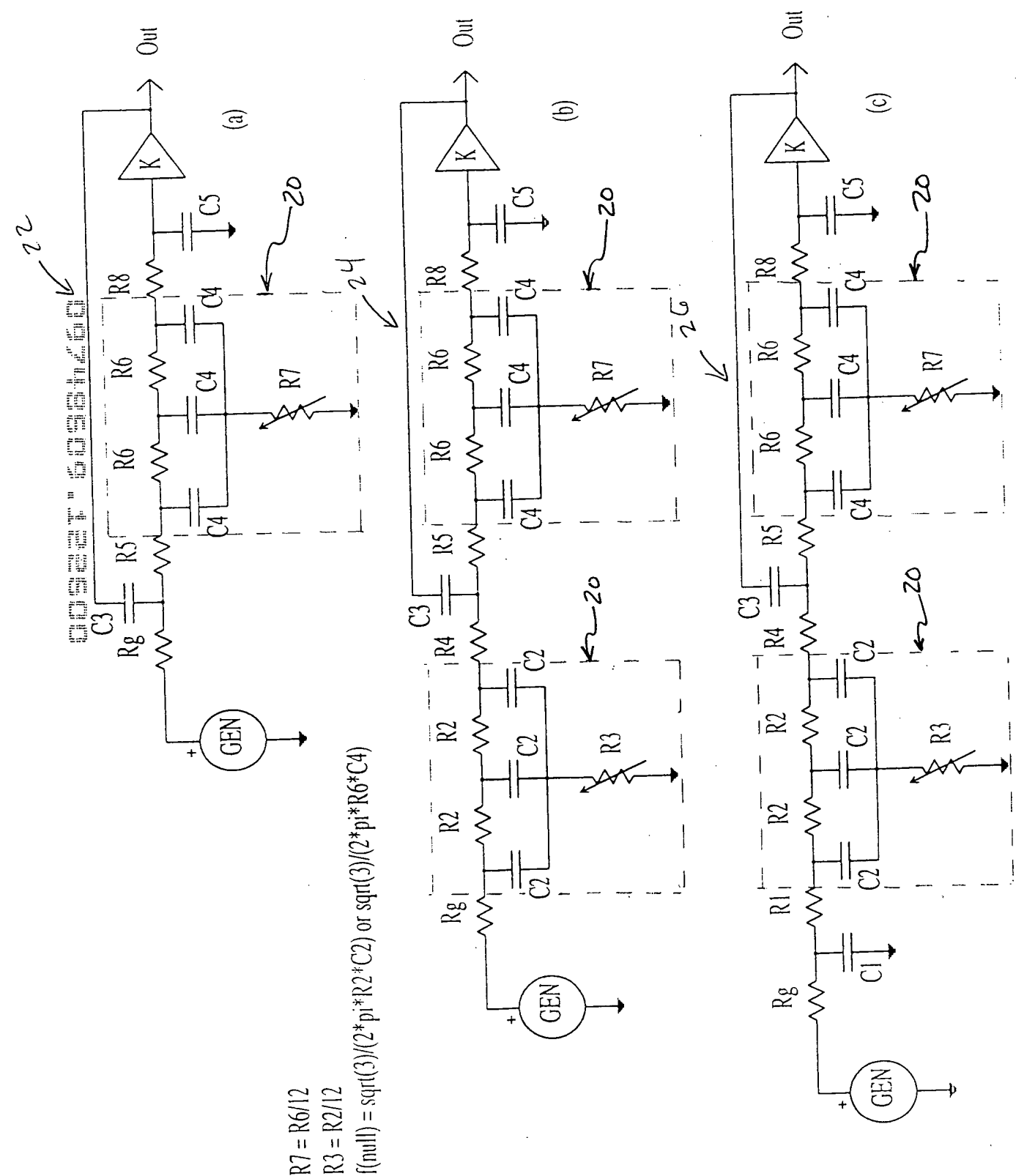

$R7 = R6/12$
 $R3 = R2/12$
 $f(\text{null}) = \sqrt{3}/(2 \cdot \pi \cdot R2 \cdot C2) \text{ or } \sqrt{3}/(2 \cdot \pi \cdot R6 \cdot C4)$

Figure 2

Low-Pass Sallen & Key Filters w Isolated Integrator Traps

Page 3 of 5

```
-----db(all.vo)
```


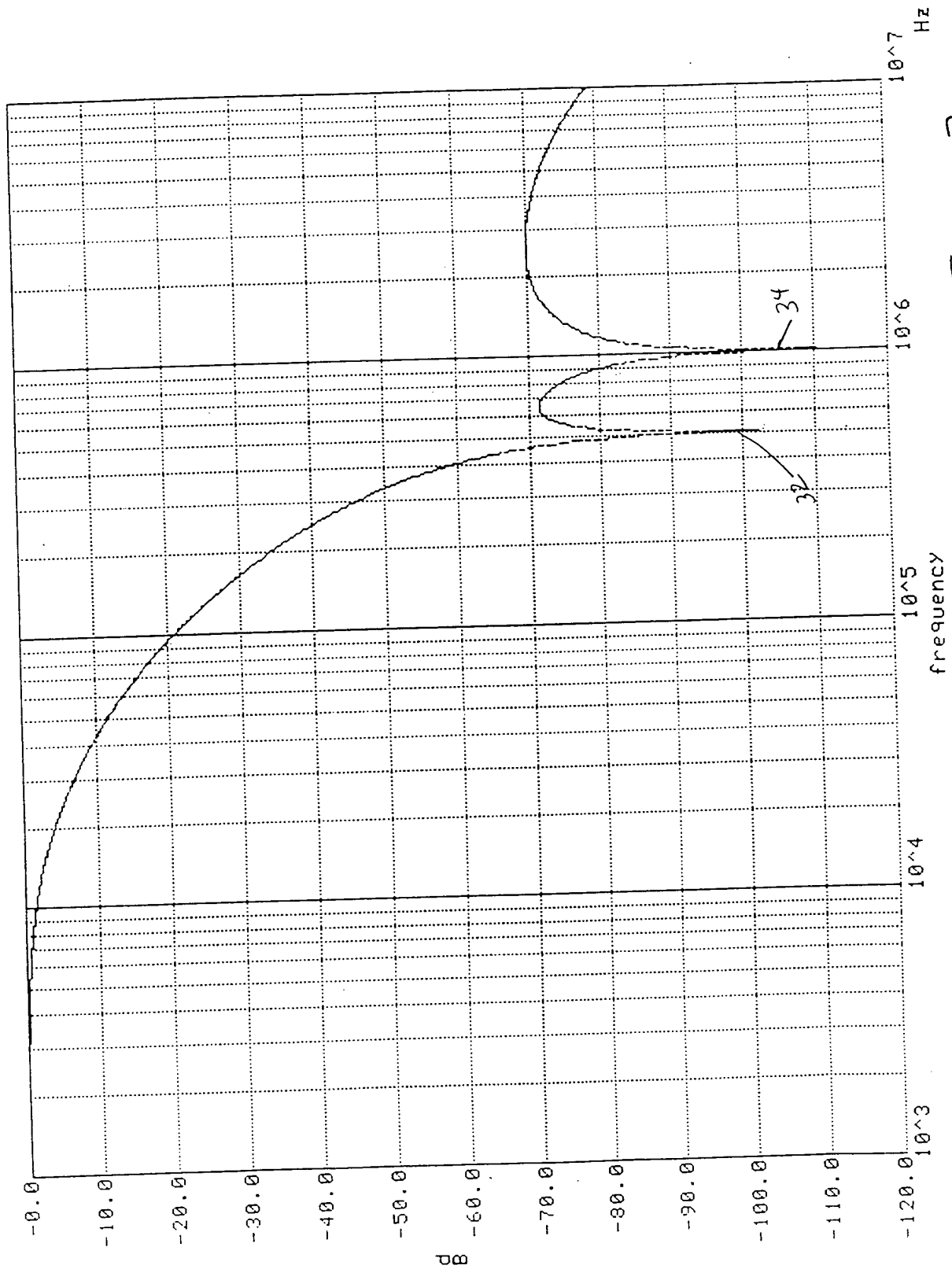


Figure 3

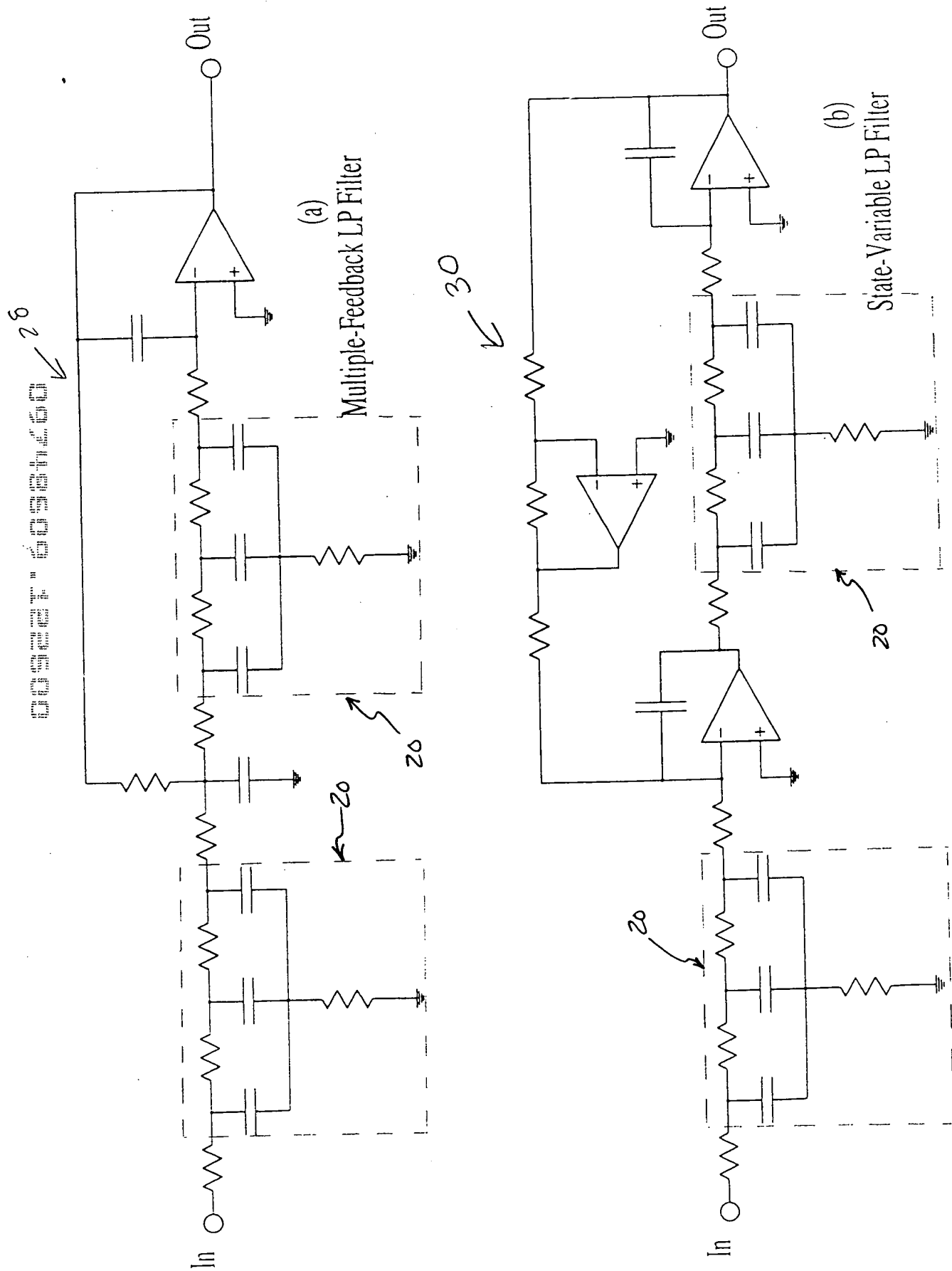

Low-Pass Filters with Isolated-Integrator Notch Filters

Figure 4

Figure 5

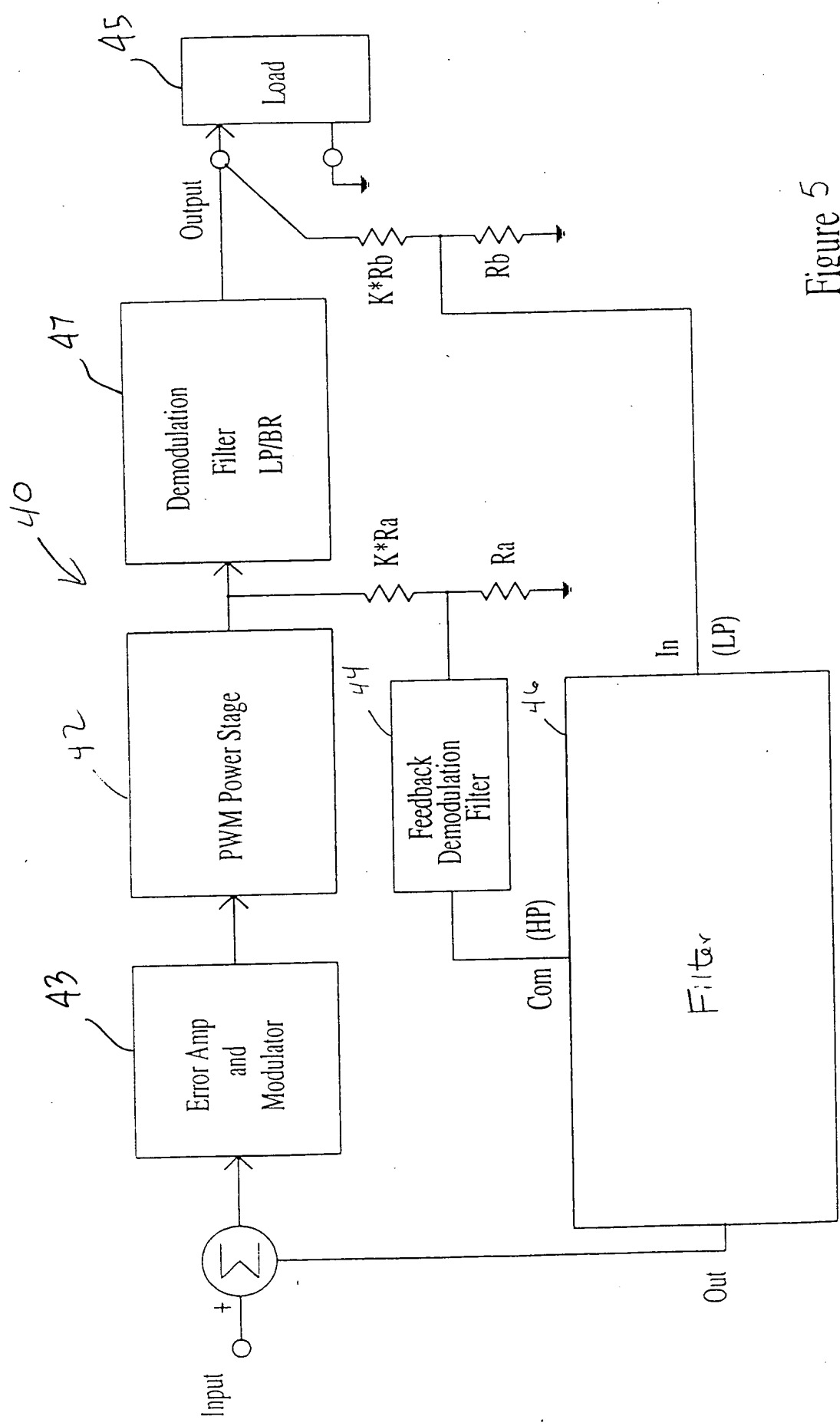


Figure 5